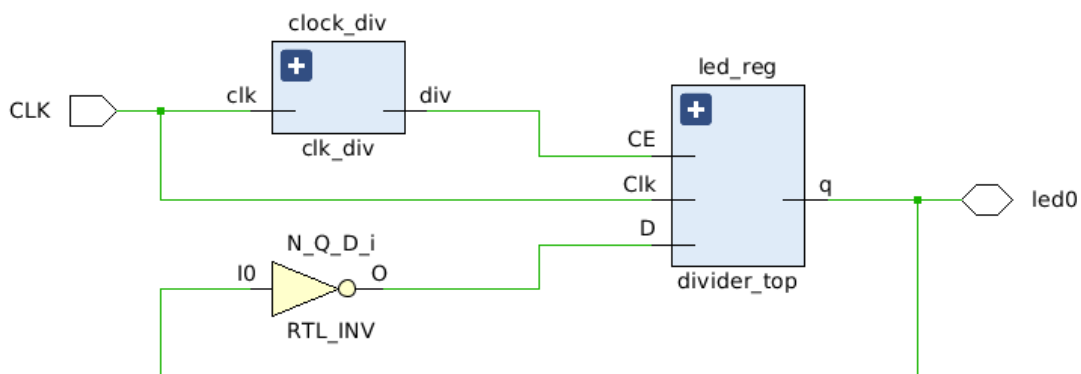



## Humble Counter

- o Embedded Systems
- o Lab Report #1
- o Fareen Pourmousavian
- o 2/28/19
- Purpose
  - o The purpose of this lab is to understand the humble counter. It uses a high frequency input clock which is slowed down and used to drive a bidirectional counter.
- For Each Part
  - o Theory of Operation
    - ♣ Given a value using the switches, the leds should light up in a way that shows the value getting incremented or decremented.
    - ♣ Initially I'm expecting it not to work and obviously have to go back and debug but assuming all goes well, then I can change the switches and load in the value and have the counter increment or decrement the counter when I press the corresponding buttons.
  - o Schematic Diagram (as desired)

### Divider\_top



## Counter\_top

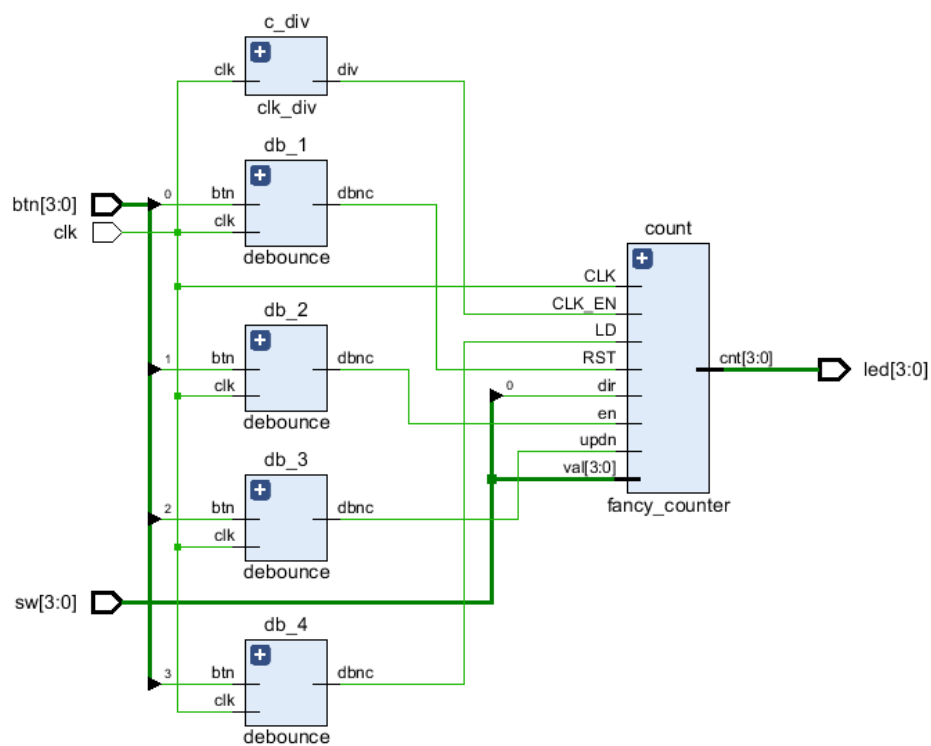

## o Design

Library IEEE;

use IEEE.std\_logic\_1164.all,IEEE.numeric\_std.all;

```

entity divider_top is
port(Clk,CE,D : in std_logic;
      q :out std_logic);
end divider_top;

architecture div_top of divider_top is
signal tmp : std_logic;
begin

    process(Clk)
    begin
        if(rising_edge(clk)) then
            if(CE = '1') then
                Q<=Not(D);
            else
                Q<= D;
            end if;
        end if;
    end process;
end div_top;

```

```

Library IEEE;
use IEEE.std_logic_1164.all,IEEE.numeric_std.all;

```

```

entity crt_1 is
port(CLK :in std_logic;
      led0 :inout std_logic);
end crt_1;

```

architecture crt\_1\_sim of crt\_1 is

component divider\_top

port(Clk,CE,D : in std\_logic;

q :out std\_logic);

end component;

component clk\_div

port(clk :in std\_logic;

div :out std\_logic);

end component;

signal div\_out, Q\_D,N\_Q\_D : std\_logic;

begin

N\_Q\_D <=NOT(led0);

clock\_div : clk\_Div

port map(CLK=>clk,

div=>div\_out);

led\_reg : divider\_top

port map(Clk=>clk,

CE=>div\_out,

D=>N\_Q\_D,

Q=>led0);

end crt\_1\_sim;

library IEEE;

```
use ieee.std_logic_1164.all, ieee.numeric_std.all;
```

entity debounce is

```
port (clk : in std_logic;
      btn : in std_logic;
      dbnc : out std_logic);
end debounce;
```

architecture deb of debounce is

```
signal counter : std_logic_vector(22 downto 0);
signal btn_reg : std_logic_vector(1 downto 0);
begin
```

```
    process(clk)
    begin
        if(rising_edge(clk)) then
            btn_reg(0)<=btn; --bit 0 gets 1
            btn_reg(1)<=btn_reg(0); --update bit 1 with bit 0 value
            if(btn_reg(1)='1') then --if bit 1 is a 1 increment counter
                counter<=std_logic_vector(unsigned(counter)+1);
                if(unsigned(counter)<2500000) then
                    dbnc<='0';
                else
                    dbnc<='1';
                end if;
            else--btn(1)==0
                counter<=(others=>'0');
                dbnc<='0';
            end if;
        end if;
    end process;
```

```
        end if;
    end if; --end if button pressed or not
end process;
end deb;
```

```
library ieee;
use ieee.std_logic_1164.all, ieee.numeric_std.all;
```

```
entity clk_div is
port(clk :in std_logic;
     div :out std_logic);
end clk_div;
```

```
architecture clk of clk_div is
signal counter : std_logic_vector (25 downto 0) := (others => '0');
begin
    process(clk)
    begin
        if(rising_edge(clk)) then
            if(unsigned(counter)<62499999) then
                counter <= std_logic_vector(unsigned(counter)+1);
                div <= '1';
            else
                counter <= (others => '0');
                div <= '0';
            end if;
            if (unsigned(counter) = 31250000) then
```

```

        div <= '1';

    else
        div <= '0';
    end if;
end if;
end process;
end clk;

```

```

library IEEE;
use ieee.std_logic_1164.all, ieee.numeric_std.all;

```

```

entity fancy_counter is
port(CLK,CLK_EN,LD,RST,dir,en,updn : in std_logic;
    val :in std_logic_vector(3 downto 0);
    cnt :out std_logic_vector(3 downto 0));
end fancy_counter;

```

```

architecture fc of fancy_counter is
signal count, count_d : std_logic_vector(3 downto 0) := (others=>'0');
signal direction : std_logic;
begin
    process(CLK)
    begin
        if( rising_edge(clk) and en='1')then
            if(rst='1')then
                cnt<= (others=> '0');
            end if;

```

```

if(clk_en='1') then
    if(ld='1') then
        count<=val;
        count_d<=count;
        cnt<=count;
    end if;
    if(updn='1')then
        direction<=dir;  --put dir into direction register
        if(direction='1') then --if direction is 1 then it counts up
            count<=std_logic_vector(unsigned(count)+1);
            cnt<=count;
            if(count=val) then --if you counted up to value reset
                count<=(others=>'0');
            end if;
        elsif(direction='0') then --if direction is 0 then it counts down
            count<=std_logic_vector(unsigned(count)-1);
            cnt<=count;
            if(count = "0000") then --if counting down reset back to original
                count<=count_d;
                cnt<=count;
            end if;
        end if;
    end if;
end if;
end process;

end fc;

```



```

library IEEE;
use ieee.std_logic_1164.all, ieee.numeric_std.all;

entity crkt_1 is
port(btn, sw :in std_logic_vector(3 downto 0);
      clk :in std_logic;
      led :out std_logic_vector(3 downto 0));
end crkt_1;

architecture crkt_sim of crkt_1 is

component debounce
port (clk : in std_logic;
      btn : in std_logic;
      dbnc : out std_logic);
end component;

component clk_div
port(clk :in std_logic;
      div :out std_logic);
end component;

component fancy_counter
port(CLK,CLK_EN,LD,RST,dir,en,updn : in std_logic;
      val :in std_logic_vector(3 downto 0);
      cnt :out std_logic_vector(3 downto 0));
end component;

```

```
signal db1_rst, db2_en, db3_upd, db4_ld, cl_div_cl_en : std_logic;
```

```
begin
```

```
db_1 : debounce
```

```
port map(clk=> clk,
```

```
        btn=> btn(0),
```

```
        dbnc=>db1_rst);
```

```
db_2 :debounce
```

```
port map(clk=> clk,
```

```
        btn=> btn(1),
```

```
        dbnc=>db2_en);
```

```
db_3 :debounce
```

```
port map(clk=> clk,
```

```
        btn=> btn(2),
```

```
        dbnc=>db3_upd);
```

```
db_4 :debounce
```

```
port map(clk=> clk,
```

```
        btn=> btn(3),
```

```
        dbnc=>db4_ld);
```

```
c_div : clk_div
```

```
port map(clk=> clk,
```

```
        div=>cl_div_cl_en);
```

```
count : fancy_counter
```

```
port map(CLK=>clk,
```

```
        CLK_EN=>cl_div_cl_en,
```

```
        LD=>db4_ld,
```

```
        RST=>db1_rst,
```

```

dir=>sw(0),
en=>db2_en,
updn=>db3_upd,
val(3)=>sw(3),
val(2)=>sw(2),
val(1)=>sw(1),
val(0)=>sw(0),
cnt(3) =>led(3),
cnt(2) =>led(2),
cnt(1) =>led(1),
cnt(0) =>led(0));
end crkt_sim;

o Test
    ♣ Test bench VHDL (not sure if required)

    Clock_divider test bench

    Library IEEE;
    use IEEE.std_logic_1164.all,IEEE.numeric_std.all;

    ENTITY Tb_clock_div IS
    END Tb_clock_div;

    architecture behave of Tb_clock_div is
    Component clock_Divider
    port(clk :in std_logic;
        led0 :out std_logic;
        clk_out :out std_logic_vector(24 downto 0));
    end Component;

```

```
signal clk : std_logic := '0';
```

```
signal led0 : std_logic;
```

```
signal clk_out : std_logic_vector(24 downto 0);
```

```
constant clk_period : time := 10 ns;
```

```
begin
```

```
uut: clock_Divider PORT MAP (
```

```
clk => clk,
```

```
led0 => led0,
```

```
clk_out => clk_out);
```

```
clk_process :process
```

```
begin
```

```
clk <= '0';
```

```
wait for clk_period/2;
```

```
clk <= '1';
```

```
wait for clk_period/2;
```

```
end process;
```

```
stim_proc: process
```

```
begin
```

```
wait for 100ns;
```

```
wait for clk_period*10;
```

```
wait;
```

```
end process;
```

```
end;
```

DebounceTest bench

Library IEEE;

use IEEE.std\_logic\_1164.all,IEEE.numeric\_std.all;

ENTITY deb\_t IS

END deb\_t;

architecture behave of deb\_t is

Component debounce

port(clk :in std\_logic;

    btn :in std\_logic;

    dbnc :out std\_logic);

end Component;

signal clk\_test : std\_logic := '0';

signal btn\_test : std\_logic;

signal dbnc\_test : std\_logic;

constant clk\_period : time := 10 ns;

begin

uut: debounce PORT MAP (

clk => clk\_test,

btn => btn\_test,

dbnc => dbnc\_test);

clk\_process :process

```

begin
    clk_test <= '0';
    wait for clk_period/2;
    clk_test <= '1';
    wait for clk_period/2;

```

```

end process;

```

```

stim_proc: process

```

```

begin

```

```

    wait for 100ns;

```

```

    btn_test<='1';

```

```

    wait;

```

```

    end process;

```


```

end;

```

♣ simulation results (screen shots)


Debounce

 

 
## Clock divider test bench




o Implementation (If required to demo on board)



♣ Vivado

 


Elaboration Schematic

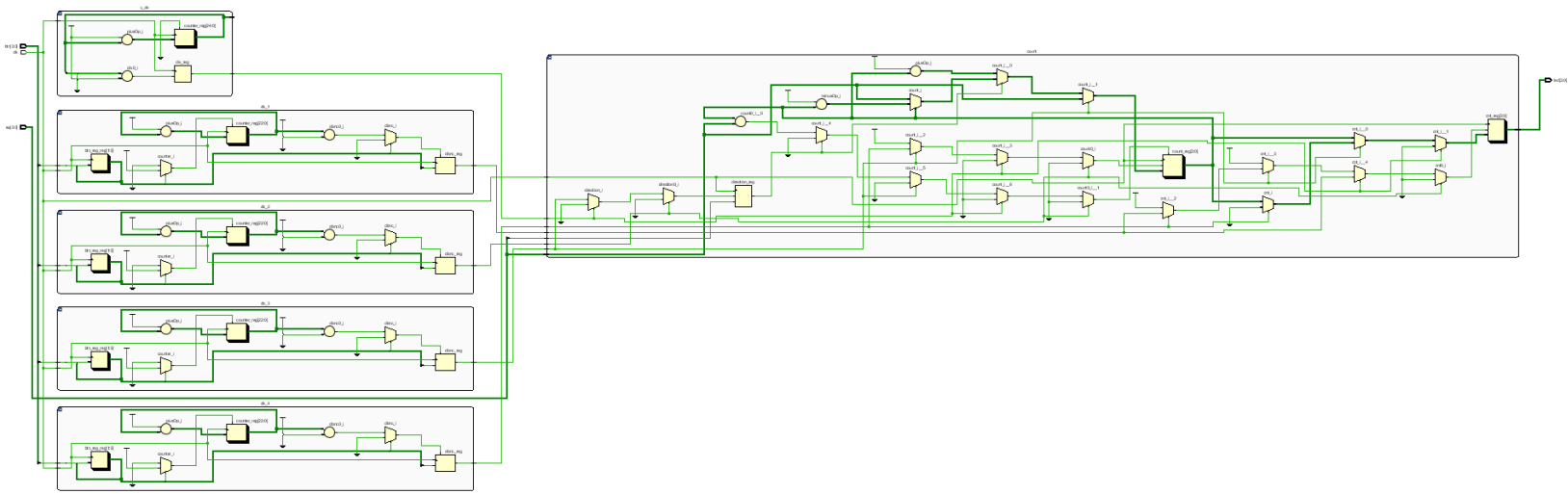


♣ Vivado Synthesis Schematic

Counter\_Top



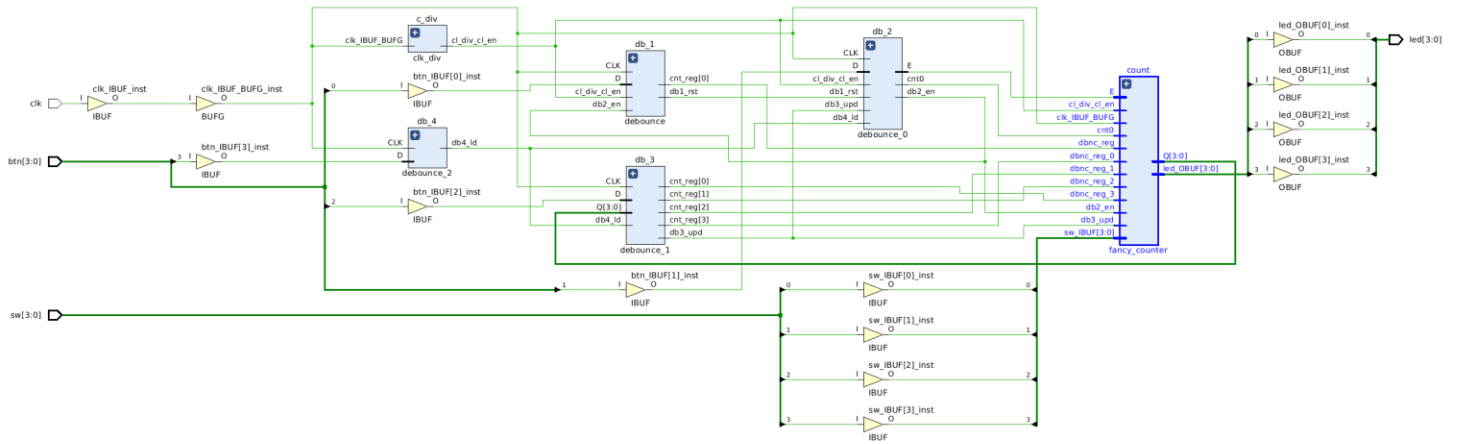


Divider\_top(not sure if needed)

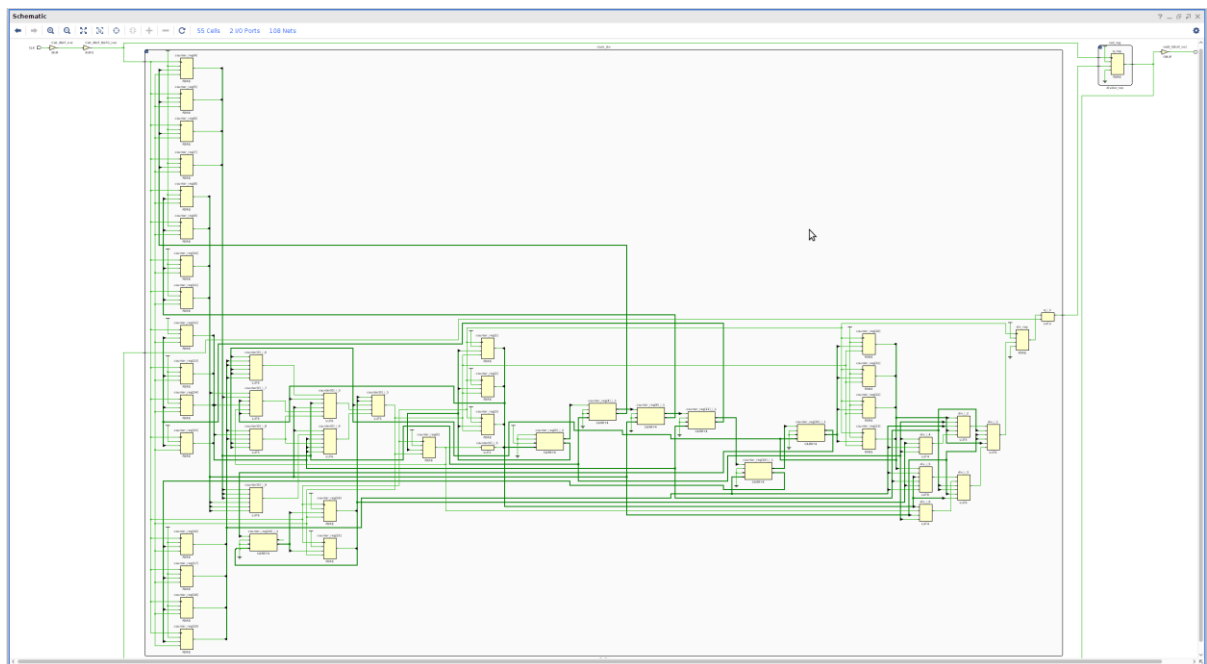

♣ Vivado Project Summary Images


• Post-Synthesis Utilization Table

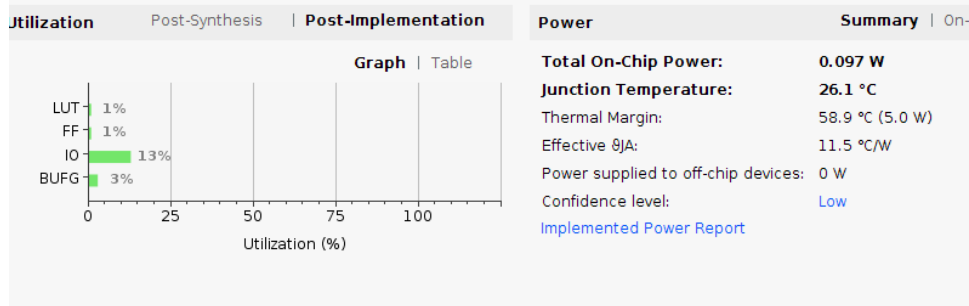
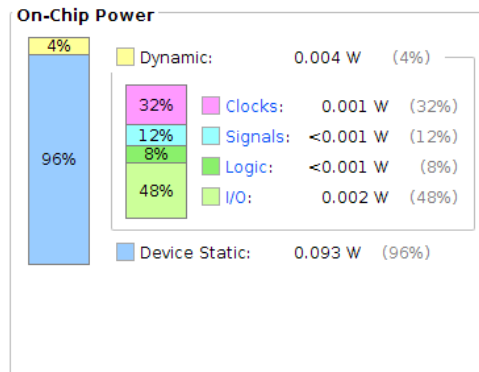
### • On-chip Power Graphs

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

**Total On-Chip Power:** 0.097 W  
**Design Power Budget:** Not Specified  
**Power Budget Margin:** N/A  
**Junction Temperature:** 26.1°C  
 Thermal Margin: 58.9°C (5.0 W)  
 Effective  $\theta_{JA}$ : 11.5°C/W  
 Power supplied to off-chip devices: 0 W  
 Confidence level: Low  
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



### ♣ ZYBO\_Master.xdc

• The only things that needed to be changed was the uncommenting of all the LED, Switches, buttons and clock signals so that those ports on the board would work when I try to implement my design on the board.

### • Discussion

o Q1.1: We need 62500000

o Q1.2: it requires 26 bits because if we do Log base 2 of 62500000 we get 25.8.. which rounds up to 26 bits

o Q2.1: The value of the button bounces between 1 and 0 until it stabilizes

o Q2.3: We need 2500000 ticks

o Q2.4: We would require 22 bits since the log base 2 of 2500000 is 21.2... we must round up and use 22 bits.

o Observations / Discoveries

♣ I actually learned how to code in behavioral and be able to combine those parts because I thought I had to code it all in structural so that I can connect everything together but actually I can make separate files and make components that refer to those entities and will do the same thing. I also learned that lab instructions are confusing and will need to re-read every task due to the convoluted directions.

o Questions / Follow Up

♣ I understand most of the things that were asked of me. The lab manual was a bit confusing to a degree where it took me around 20 minutes to understand that in part 1 the divider\_top was asking for a D-Flip-Flop. The debouncer image in the manual was a bit confusing because what they were asking was the opposite of what the diagram was showing. I initially thought that we only needed to see that it was a logic '1' for 4 consecutive times but after talking to the teaching assistants that was cleared up.

♣ The only thing I'm not 100% confident in is making test benches in general. That is the thing that took me a long time to figure out. Then I realized that once you make one test bench, other test benches use a similar format.